

# Thor Arm Hardware Wiring Diagram

This guide provides a detailed circuit diagram and explanation for wiring the physical hardware of the Thor robot arm. This setup uses a Raspberry Pi for high-level control (ROS 2) and an Arduino Mega for real-time motor and encoder processing.

**IMPORTANT:** Always disconnect all power sources (both USB and the main DC power supply) before making or changing any connections.

## System Overview Diagram

This diagram shows the high-level connections between all the major components.

## Detailed Wiring Instructions

Follow these steps carefully. It is crucial to connect the grounds correctly to avoid damaging your components.

### 1. Power Distribution

You have two separate power circuits: one for the logic (Pi & Arduino) and one for the high-power motors. They must share a common ground.

- **Motor Power (5V 10A DC Supply):**
  - Connect the **Positive (+)** terminal of the 5V 10A power supply to the **VM+** (or **VCC**) pin on all three **TB6612FNG motor driver** boards.
  - Connect the **Negative (-)** terminal (Ground) of the 5V 10A power supply to the **GND** pin on all three **TB6612FNG motor driver** boards.
- **Logic Power (Raspberry Pi):**
  - The Raspberry Pi is powered by its own 5V 3A USB-C adapter.
  - The Arduino Mega will be powered by the Raspberry Pi via the USB cable.
- **CRITICAL - Common Ground:**
  - Run a single jumper wire from any **GND** pin on the **Arduino Mega** to the **Negative (-)** terminal bus of your motor power supply (or any GND pin on one of the motor drivers). **This is the most important connection.** Without it, the control signals from the Arduino will not work correctly.

### 2. Control Connection (Raspberry Pi to Arduino)

- Connect the **Raspberry Pi** to the **Arduino Mega** using a standard USB-A to USB-B cable. This single cable provides both power to the Arduino and the serial data connection.

### 3. Motor and Driver Connections (Arduino to Motors)

You will need three TB6612FNG driver boards. Each board controls two motors (Motor A and Motor B).

- **For each of the 6 motors:**

- Connect the two motor leads to the A01/A02 (for Motor A) or B01/B02 (for Motor B) terminals on a driver board.
- Connect the **PWM** pin from the Arduino (e.g., Pin 2 for Joint 1) to the PWMA (or PWMB) pin on the driver board.
- Connect two digital pins from the Arduino (e.g., Pins 22 and 23 for Joint 1) to the AIN1/AIN2 (or BIN1/BIN2) pins on the driver board. These control the motor's direction.
- Connect the motor driver's STBY (Standby) pin to an Arduino digital pin (e.g., Pin 8). You can connect all three STBY pins together and control them with a single Arduino pin. This pin must be set to HIGH to enable the drivers.

#### 4. Encoder Feedback Connections (Motors to Arduino)

Each goBILDA motor has a 6-pin encoder cable.

- **For each of the 6 encoders:**

- **+ (VCC):** Connect this to the **5V** pin on the Arduino.
- **- (GND):** Connect this to any **GND** pin on the Arduino.
- **A (Channel A):** Connect this to an **interrupt-capable** digital pin on the Arduino Mega (e.g., Pin 18).
- **B (Channel B):** Connect this to any other digital pin on the Arduino Mega (e.g., Pin 19).

Why Interrupt Pins?

The Arduino Mega has specific pins that can trigger interrupts (Pins 2, 3, 18, 19, 20, 21). Using these for Channel A of each encoder guarantees that the Arduino will never miss a pulse, ensuring your position tracking is perfectly accurate. Refer to an Arduino Mega pinout diagram to identify all interrupt pins.

After completing this wiring, your next step will be to upload the `thor_firmware.ino` sketch to the Arduino, making sure to update the pin definitions in the code to match the physical connections you just made.